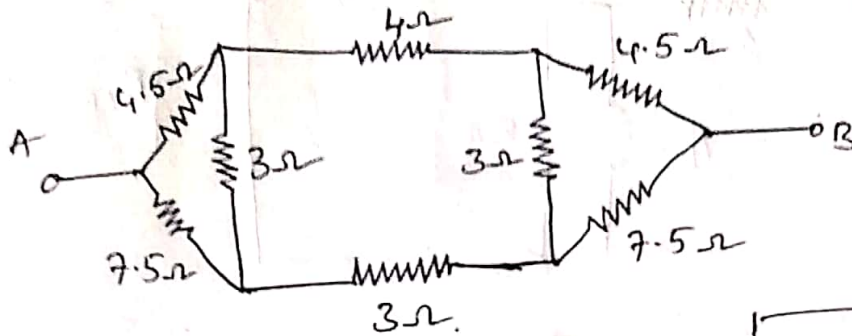



Assignment -1

1. Find an equivalent resistance between A and B




Ans: $R_{AB} = 7.45\Omega$

2.

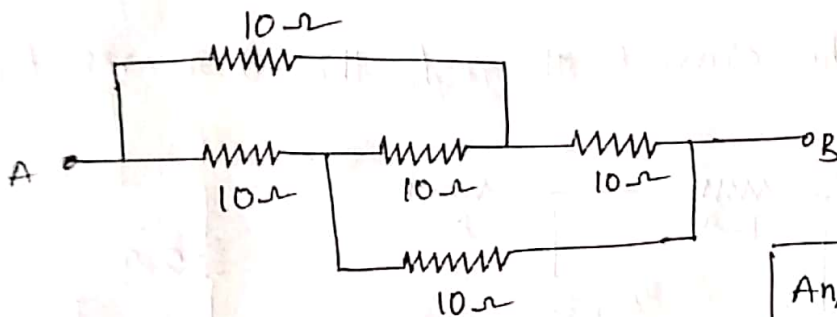


Ans: 10Ω

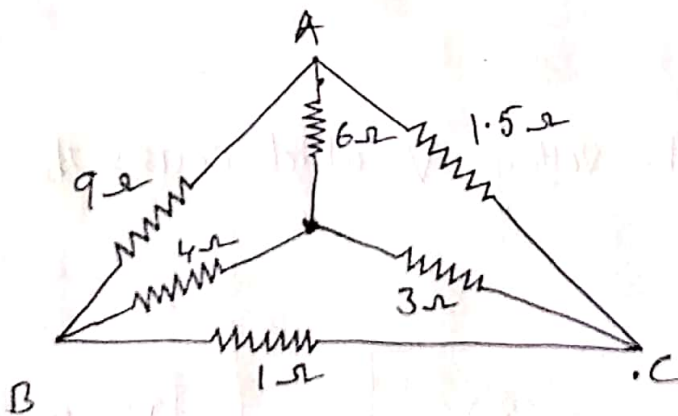3. Find an equivalent resistance b/w A and B




$R_{AB} = 1.64\Omega$

4.

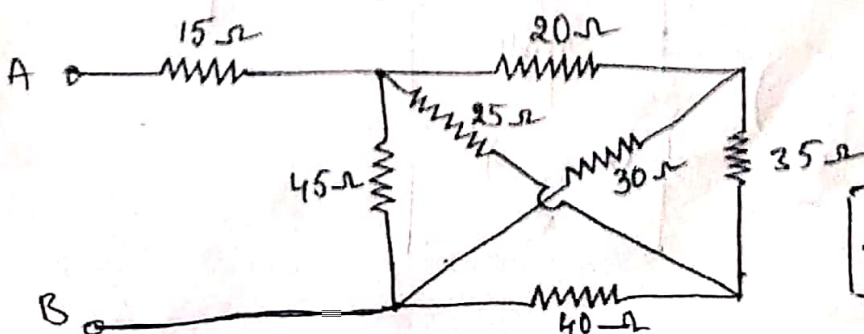


$R_{AB} = 32.36\Omega$

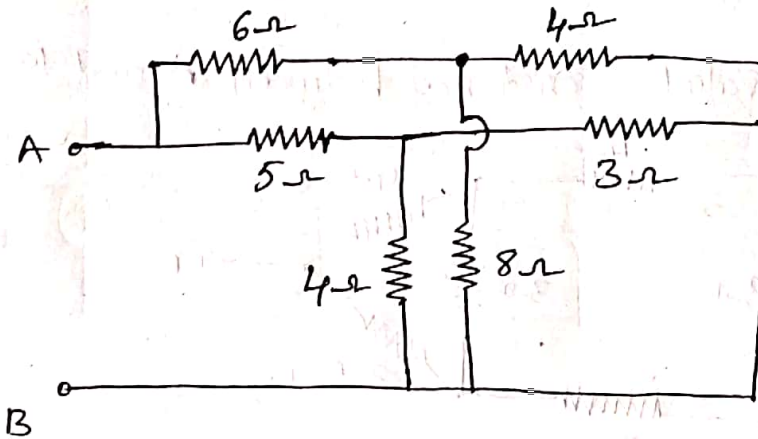⑤. Find an equivalent resistance b/w A and B




$$R_{AB} = 3.78\Omega$$

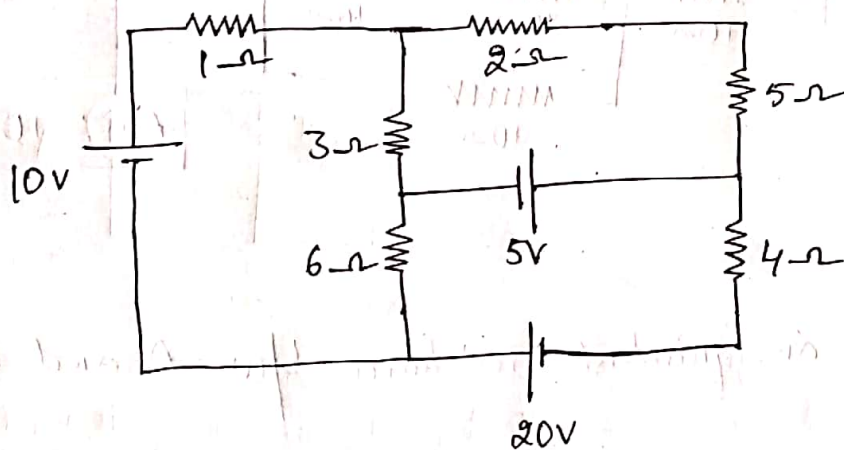⑥. Find the current through the 5Ω resistor.




$$I_{5\Omega} = 0.78A$$

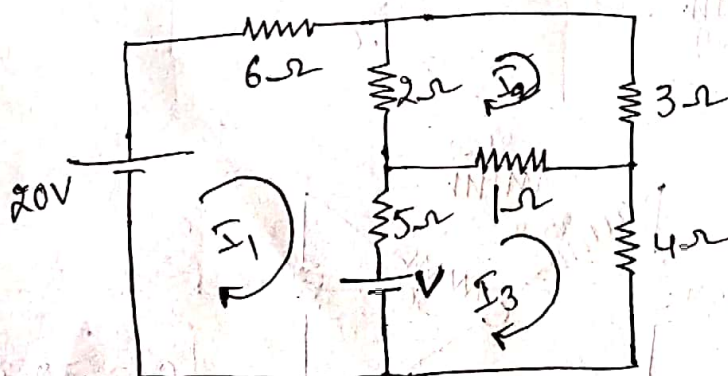⑦. Determine the voltage 'V' which causes the current I_1 to be zero.




$$V = 43.7V$$

8. Find the current in the 5Ω resistor.

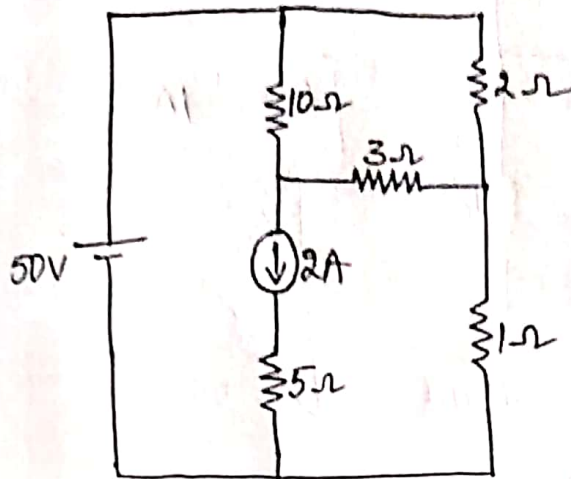

Ans:- 4.67 A

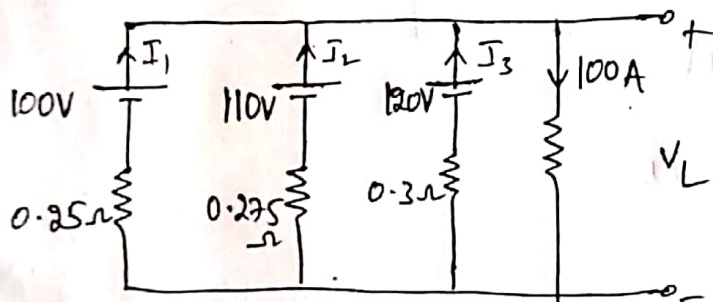9. Find the current supplied by each battery and Load voltage



Ans:-


$$I_1 = 1.08\text{ A}$$

$$I_2 = -35.38\text{ A}$$

$$I_3 = -65.77\text{ A}$$

$$V_L = 100.27\text{ V}$$


10. Find V_1 and V_2

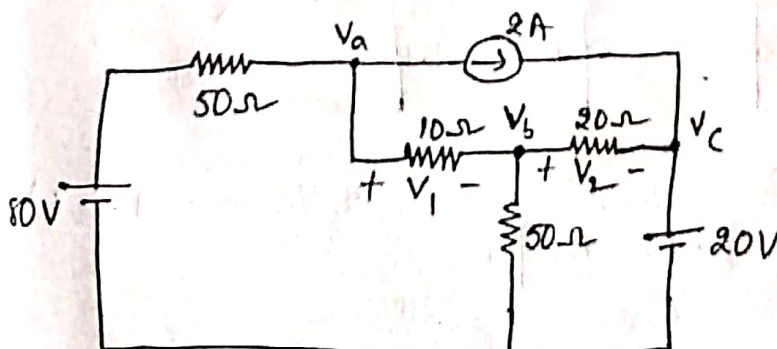

$$V_1 = -4.61\text{ V}$$


$$V_2 = -12.31\text{ V}$$

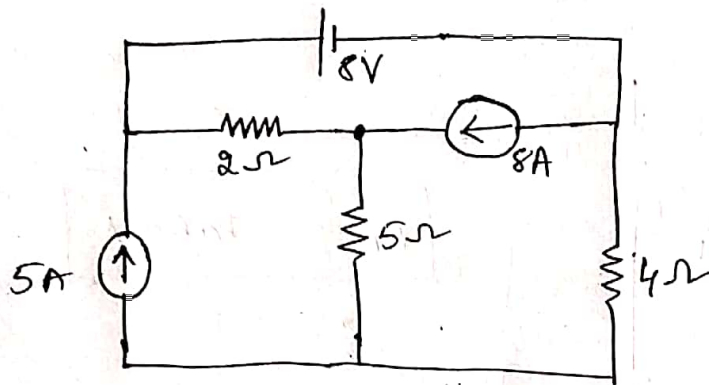⑪. find the current through the 4Ω resistor




Ans: 1A

⑫. Find the voltage V_{AB}

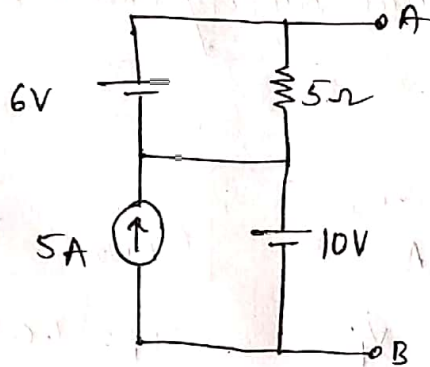


$V_{AB} = 16V$

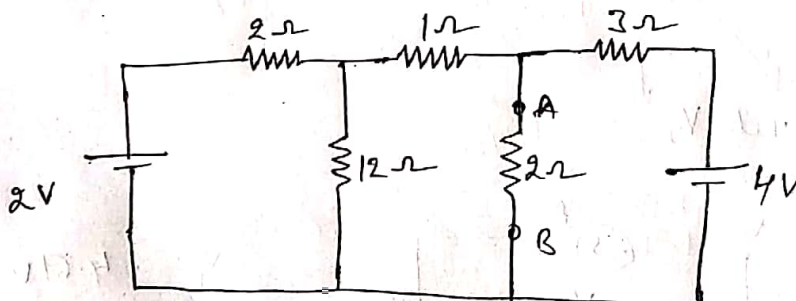⑬. Find the current through the 2Ω resistor by using Thevenin's Theorem.




Ans:- 0.82 A

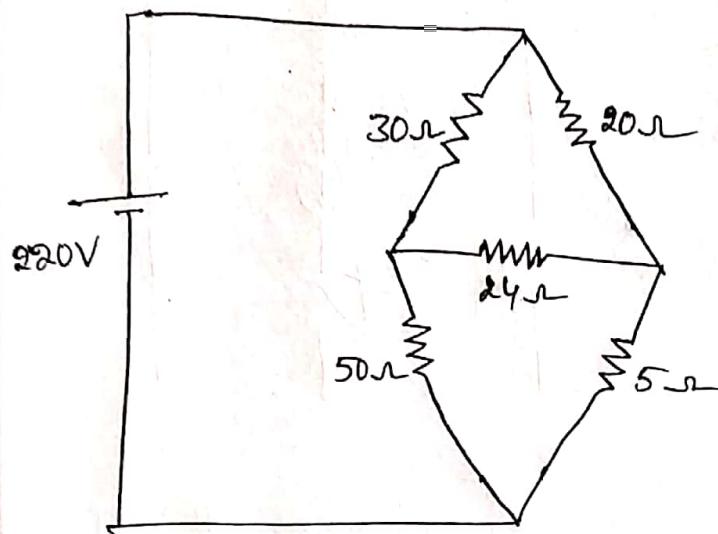- (14). By applying Thevenin's theorem, determine the current through the $24\ \Omega$ resistor.



Ans:- 2 A

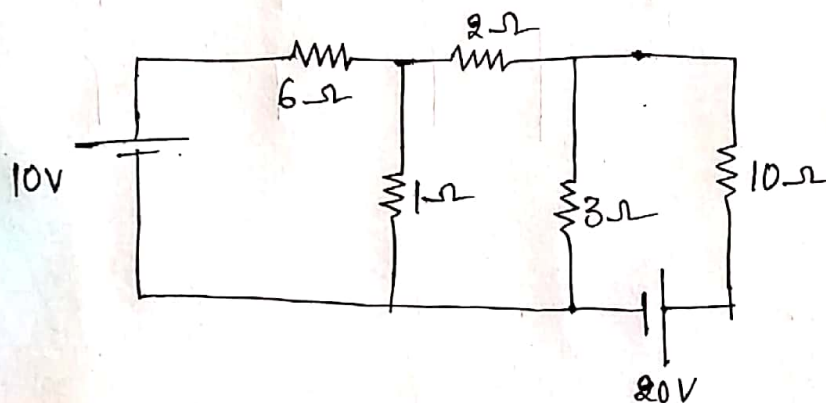- (15). Apply Norton's theorem to find the current through the $10\ \Omega$ resistor.



Ans: 1.68 A